

# CURRENT ELECTRICITY




DATE \_\_\_\_\_

PAGE \_\_\_\_\_

10/6/2023

Considering homogenous conductor

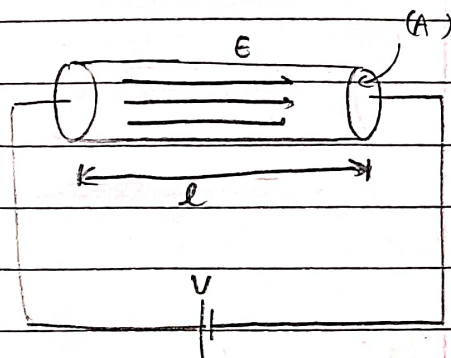

$$E = \frac{V}{l} \Rightarrow F_e = e \left( \frac{V}{l} \right)$$

$$\Rightarrow a_e = \left( \frac{e}{m} \right) \left( \frac{V}{l} \right)$$

Let  $\tau$  be the time b/w successive collisions of  $e^-$ .

Assuming  $e^-$  start from rest after every collision.

$$v = a\tau = \left( \frac{e}{m} \right) \left( \frac{V}{l} \right) (\tau)$$

$$v_{avg} = \frac{0+v}{2} \quad (\because \text{uniform acc.})$$

$$= \frac{v}{2}$$

$$v_{drift} = v_{avg} + \overset{\text{(somehow)}}{v_{\text{due to random motion}}} = \frac{v}{2} + \frac{v}{2}$$

$$= \underline{\underline{v}}$$

• Drift speed/vel. — speed with which  $e^-$  move in opp. dir<sup>n</sup> to  $E$  applied.



NOTE:  $v_d \neq$  Speed of current

When switch closed, current flows instantaneously

Let  $n$  be the # free  $e^-$ .

(Charge density) (Vol.)

In time  $dt$ ,  $dq = ne (AV_d dt)$   
pass through a certain cross section

$$i = \frac{dq}{dt} \Rightarrow \boxed{i = neAV_d}$$

$$i = neA \left( \frac{e}{m} \right) (\tau) \left( \frac{V}{l} \right) = \left( \frac{ne^2\tau}{m} \right) \left( \frac{VA}{l} \right)$$

(depends on material) (depends on Temp.) (depend on geometry of cond.)

$$R = \frac{V}{i} = \left( \frac{m}{ne^2\tau} \right) \left( \frac{l}{A} \right)$$

$$= \frac{\rho l}{A}$$

(Resistivity  
or specific resistance)

$$\boxed{\rho = \frac{m}{ne^2\tau}}$$

(Conductivity)

$$\sigma = \frac{1}{\rho}$$

(Conductivity)

$$G = \frac{1}{R}$$

Unit:  $Mho (\Omega^{-1})$

$$\frac{i}{A} = \sigma E \Rightarrow$$

$$\vec{j} = \sigma \vec{E}$$

(current density)

\* Normal to cross-sectional area

• Thermal/Temp. coeff. of Resistance ( $\alpha$ ) —


$$R = R_0(1 + \alpha \Delta T)$$

NOTE:

$\alpha > 0$  for conductors


$\alpha < 0$  for semi-conductors

Q. Find R

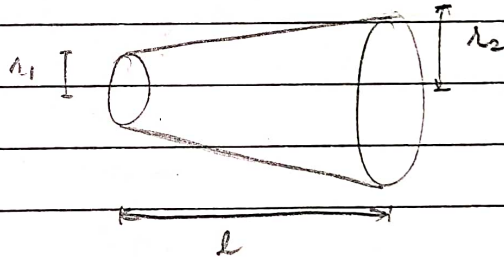

$$A. \quad dR = \frac{\rho dx}{A_x}$$
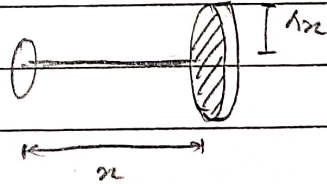
$$= \frac{\rho l^2 dx}{\pi^2 (l r_1 + (r_2 - r_1)x)^2}$$



$$r_x = r_1 + \frac{(r_2 - r_1)x}{l}$$

All elem. in series.

$$= \frac{(l-x)r_1 + x r_2}{l}$$


$$\Rightarrow R = \int dR = \int_0^l \frac{\rho l^2 dx}{\pi^2 (l r_1 + (r_2 - r_1)x)^2}$$

$$= \left( \frac{\rho l^2}{\pi^2} \right) \left( \frac{1}{r_2 - r_1} \right) \left[ \frac{1}{l r_1} - \frac{1}{l r_2} \right] = \left( \frac{\rho l}{\pi r_1 r_2} \right) **$$





Q.

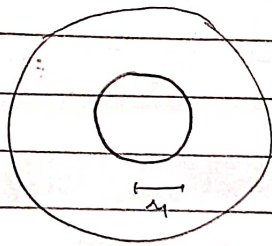

Find R.

(All elements in series)


A.

$$dR = \frac{\rho dx}{A_2} = \frac{\rho dx}{4\pi r_2^2} \Rightarrow R = \int dR$$

$$= \int_{r_1}^{r_2} \frac{\rho dx}{4\pi r^2}$$


$$= \frac{\rho}{4\pi} \left[ \frac{1}{r_1} - \frac{1}{r_2} \right]$$

Q.

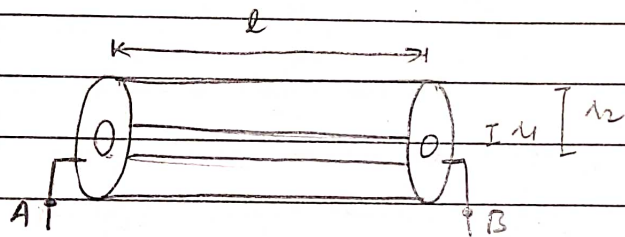

Find R.



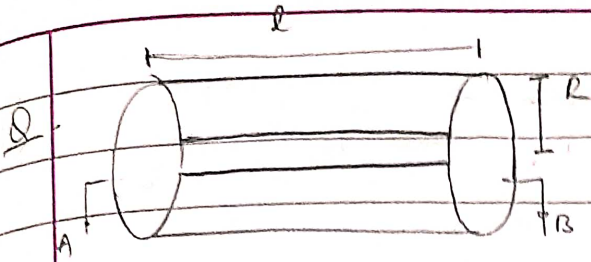

Find  $R$  if  $I = I_0 \left(1 + \frac{1}{R}\right)$

$x \rightarrow$  dist from axis of cyl.


$$A. \quad dR = \frac{I_0 x l}{A_0 x} = I_0 \left(\frac{1+x}{R}\right) \left(\frac{l}{2\pi x dx}\right)$$

All elems in  $II \Rightarrow \frac{1}{dR} = \frac{2\pi R}{I_0 l} \left(\frac{x}{R+x}\right) dx$


$$\frac{1}{R} = \int \frac{1}{dR} = \int_0^R \left(\frac{2\pi R}{I_0 l}\right) \left(1 - \frac{R}{R+x}\right) dx$$

$$= \frac{2\pi R^2}{I_0 l} [1 - \ln(2)]$$
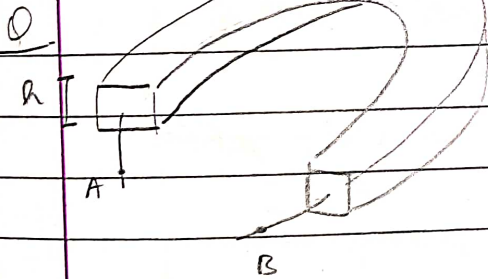
$$\Rightarrow R = \frac{I_0 l}{2\pi R^2 (1 - \ln(2))}$$




Semicircular  
find  $R$ .

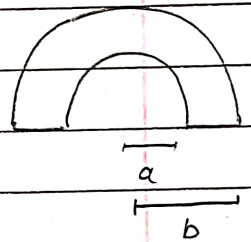

$$A. \quad dR = \frac{p(\pi x)}{h dx}$$

$$\frac{1}{R} = \int \frac{1}{dR} = \int_a^b \frac{h}{p\pi} \frac{dx}{x}$$

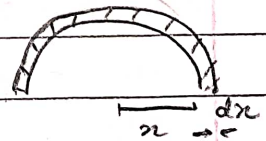
$$= \frac{h}{p\pi} \ln\left(\frac{b}{a}\right) \Rightarrow R = \frac{p\pi}{h \ln(b/a)}$$





(V maintained at ends)


Q.

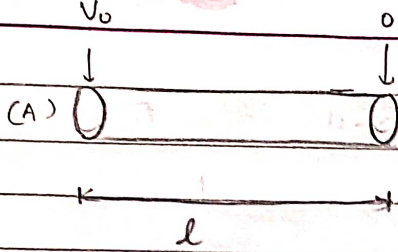

$$\rho = \rho_0 \left(1 + \frac{V}{V_0}\right)$$

Find R.

A.

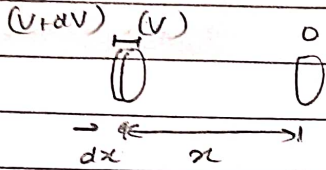

(i same through all cross sections)

$$(V+dV) - V = i \, dR$$

$$\Rightarrow dV = \frac{i \, dx}{A} \rho_0 \left(1 + \frac{V}{V_0}\right)$$

$$\Rightarrow \int_0^{V_0} \frac{dV}{V+V_0} = \int_0^l \frac{\rho_0 i}{V_0 A} dx$$


$$\Rightarrow l(R) = \frac{\rho_0 i l}{V_0 A}$$

$$\Rightarrow i = \frac{V_0 A}{\rho l} l(R) \Rightarrow R = \frac{V}{i} = \frac{\rho l}{A l(R)}$$

→ Max power transfer theorem

$$P = i^2 R$$

$$= \frac{E^2 R}{(R+r)^2}$$

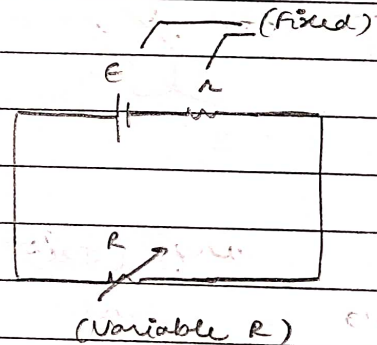


$$\frac{dP}{dR} = E^2 \frac{(R+r)^2 - 2R(R+r)}{(R+r)^4}$$

$$= E^2 \frac{(R^2 - R^2)}{(R+r)^2} = 0 \Rightarrow R = r$$

$P = P_{max}$  for  $R = r$




Q.

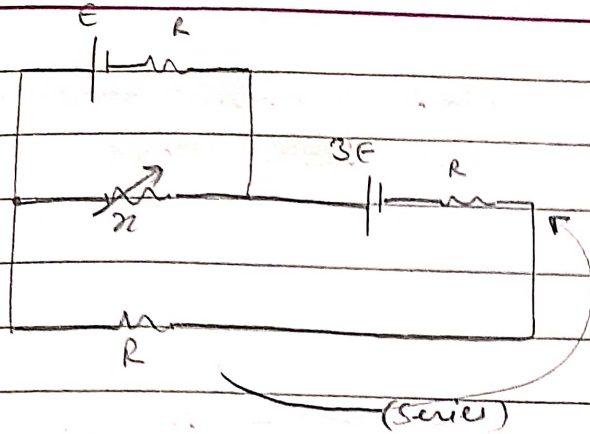

find  $x$  for which power consumed in the resistor is max.

A.

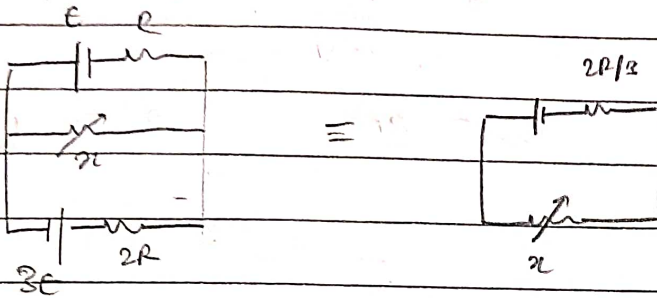

$$\Rightarrow P = P_{max}$$

$$\text{for } x = \underline{2R/3}$$

→ Heating effect of current  
(Joule's law of heating)

Power consumed by a resistor is dissipated as heat.

$$H = i^2 R t = \frac{V^2 t}{R} = i V t$$

For any load, marked voltage & marked power is given.

eg 100 W at 220 V.




load consumes 100W at 220V.

$$\Rightarrow R_{load} = \frac{(220)^2}{100} = 484 \Omega$$






(50W, 200V) (100W, 100V)

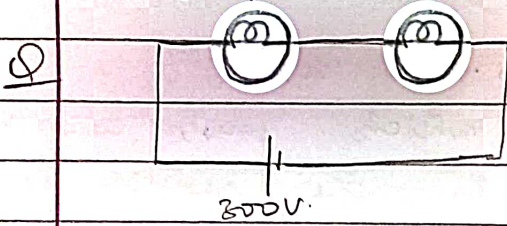

Find power consumed by each load.

A:

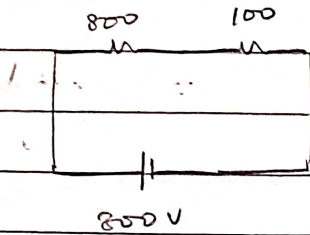

$$i = \frac{200}{900} = \frac{1}{3}$$

$$P_{800} = \frac{800}{9}$$

$$P_{100} = \frac{100}{9}$$

08/06/2023

Q. The current through resistor of resistance  $R$  is varied from 0 to  $i_0$  linearly with time from  $t=0$  to  $t=T$ . Find heat produced.

A:

$$i = \frac{i_0}{T} t$$

$$dH = i^2 R dt = \frac{i_0^2}{T^2} R t^2 dt$$

$$H = \frac{i_0^2 R (T^3)}{3T^2} = \frac{i_0^2 RT}{3}$$

Q. Total charge  $q$  is passed through resistor of resistance  $R$  in a time interval of  $t=0$  to  $t=T$ .

The current in resistor decreases linearly with time with some initial value at  $t=0$  to zero at  $t=T$ .



A. 
$$i = i_0 \left(1 - \frac{t}{T}\right)$$

$$dH = i^2 R dt$$

$$= i_0^2 R \left(1 - \frac{2t}{T} + \frac{t^2}{T^2}\right) dt$$

$$dq = i dt$$

$$= i_0 \left(1 - \frac{t}{T}\right) dt$$

$$H = i_0^2 R \left(T - \frac{T^2}{2} + \frac{T^3}{3T^2}\right)$$

$$= \frac{i_0^2 R T}{3} = \frac{4q^2 R}{3T}$$

$$q = i_0 \left(T - \frac{T^2}{2T}\right)$$

$$= \frac{i_0 T}{2}$$

Q. In the above Q, if  $i_0$  varies continuously after  $T$  time, find heat produced.

A. 
$$i = i_0 e^{-\frac{\lambda(2)t}{T}}$$

$$dH = i^2 R dt$$

$$= i_0^2 R e^{-\frac{2\lambda(2)t}{T}} dt$$

$$dq = i_0 e^{-\frac{\lambda(2)t}{T}} dt$$

$$\Rightarrow H = -i_0^2 R \left(\frac{T}{2\lambda(2)}\right) \left[e^{-\frac{2\lambda(2)t}{T}}\right]_0^\infty$$

$$q = -\frac{i_0 T}{\lambda(2)} \left[e^{-\frac{\lambda(2)t}{T}}\right]_0^\infty$$

$$= \frac{i_0^2 R T}{2\lambda(2)} = \left(\frac{q^2}{T^2}\right) \frac{\lambda(2) R T}{2\lambda(2)}$$

$$= \frac{i_0 T}{\lambda(2)}$$

$$= \frac{q^2 R \lambda(2)}{2T}$$




# ELECTRICAL INSTRUMENTS

## → Ammeter & Voltmeter


Ideal (A) — Zero resistance

Ideal (V) —  $\infty$  resistance

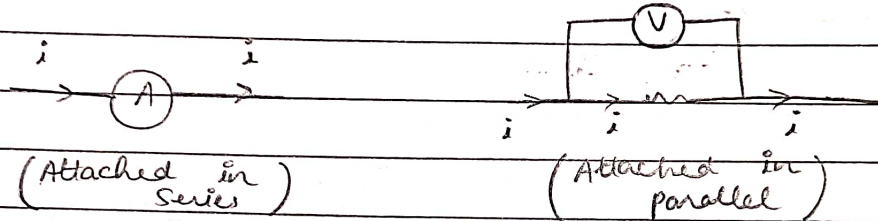

NOTE: Ammeter measures the current passing through it.

Q. If

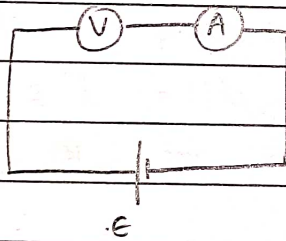


Reading

A — 0 Amp.

V — E Volt

Q. Find reading of (A)


A.  $i = \left( \frac{E}{R} \right)$

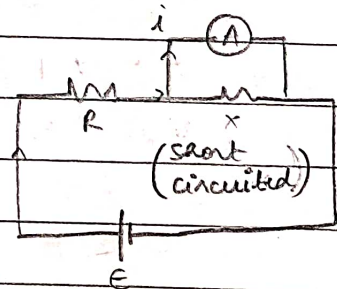





Q.

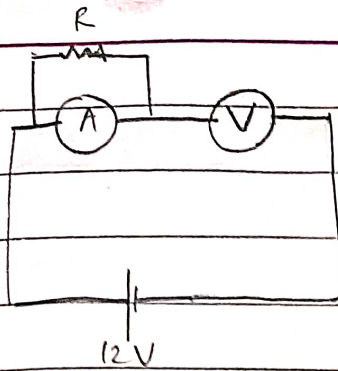

After connecting R

Readings

$$A: i_0 \rightarrow i_0/2$$

$$V: V_0 \rightarrow 2V_0$$

Find  $V_0$ 

A.


$$(ML) \quad 1. \quad i_0 R_A + V_0 = 12 \quad \leftarrow \text{(Before)}$$

$$2. \quad \frac{i_0}{2} R_A + 2V_0 = 12 \quad \leftarrow \text{(After)}$$

2

$$\Rightarrow V_0 = 4$$

Q.

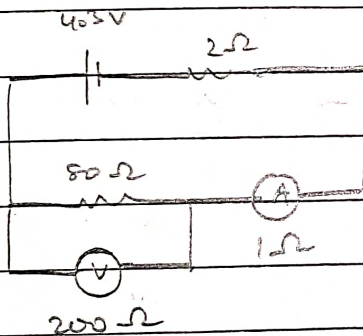

Find readings

of (A) &amp; (V)



$$A. \quad R_{eq} = 2 + 1 + \frac{50 \times 200}{250} = 4\Omega \quad \Rightarrow \quad i = 0.1$$

$$A: \quad 0.1 \text{ Amp}$$

$$V: \quad 4.3 - (0.1)(1+2) = 4 \text{ volt}$$




Polarity -

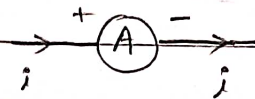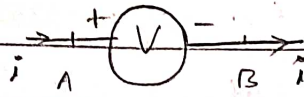

$$V_A - V = V_B$$

$$\Rightarrow V_A - V_B = V$$

Q.

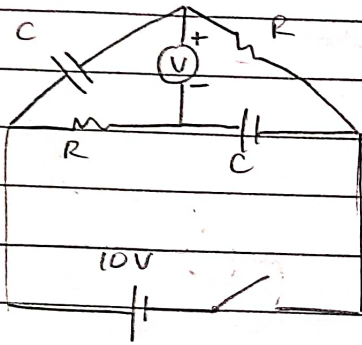


Caps initially uncharged & switch closed.



Find reading of (V) in steady-state.

Also find time after which reading is zero.

A.

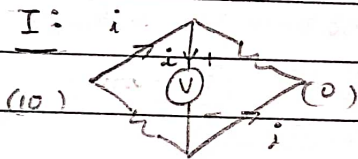

$$V_i = 10$$

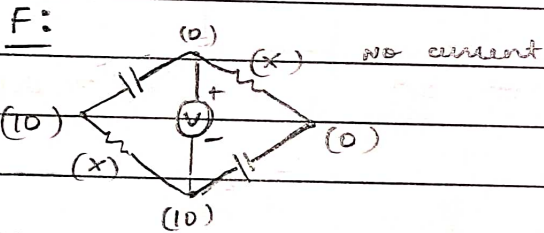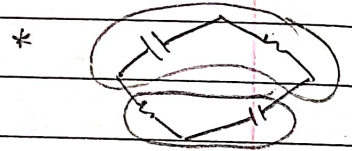

$$V_f = -10$$

These are 2 independent circuits. Hence we are able to apply RC-circuit formulae.

At time 't',  $q_{cap} = eC(1 - e^{-\frac{t}{RC}})$

$$V_{cap} = \frac{q_{cap}}{C} = e(1 - e^{-\frac{t}{RC}})$$


$$V = (10 - V_{cap}) - V_{cap}$$

$$= 10 - 2e(1 - e^{-\frac{t}{RC}})$$

$$= 20e^{-\frac{t}{RC}} - 10$$


for  $V = 0$

$$\Rightarrow t = RC \ln(2)$$

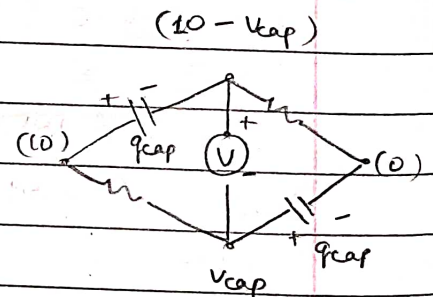


Conversion from Galvanometer -

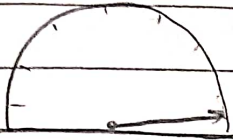Galvanometer - Device which measures current.



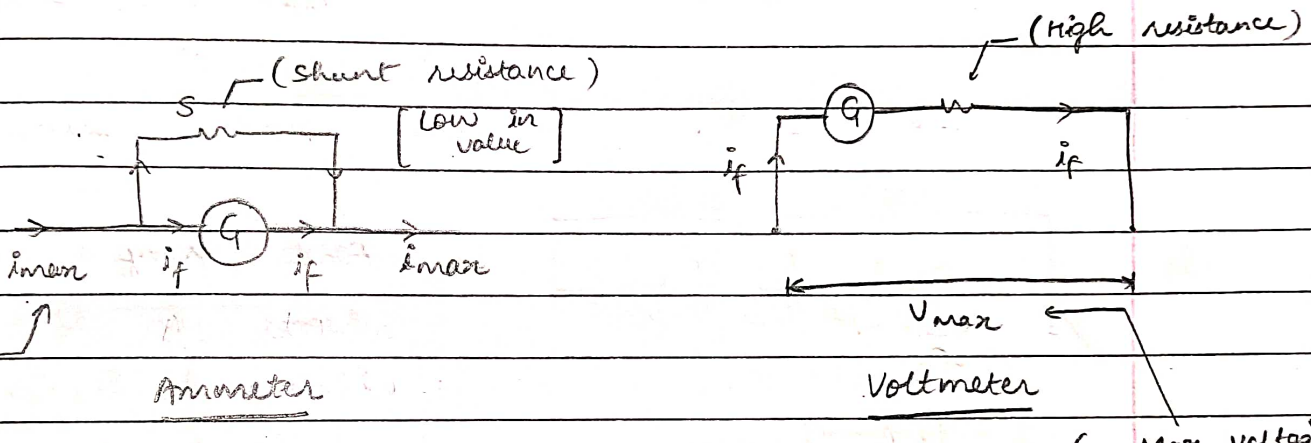Full scale deflection current ( $i_f$ )  
= (Max current measured)  
by (G)



Max i measured by (A)

Ammeter

Voltmeter

Max voltage measured by (V)

$$S(i_{max} - i_f) = G i_f$$

$$i_f (G + R_H) = V_{max}$$

$$\Rightarrow S = \frac{G i_f}{(i_{max} - i_f)}$$

$$R_H = \frac{V_{max} - G i_f}{i_f}$$

We choose S &  $R_H$  in such a manner so as to ensure only  $i_f$  passes through (G)




Q

$G = 25 \Omega \quad \& \quad i_f = 10^{-3} \text{ A}$

Find a) S for (A) with  $i_{\text{max}} = 10 \text{ A}$ b)  $R_H$  for (V) with  $V_{\text{max}} = 100 \text{ V}$ A

$$1. \quad S = \frac{(25)(10^{-3})}{(10 - 10^{-3})} \sim \underline{2.5 \times 10^{-3} \Omega}$$

$$2. \quad R_H = \frac{100 - 100}{10^{-3}} \sim \underline{10^5 \Omega}$$

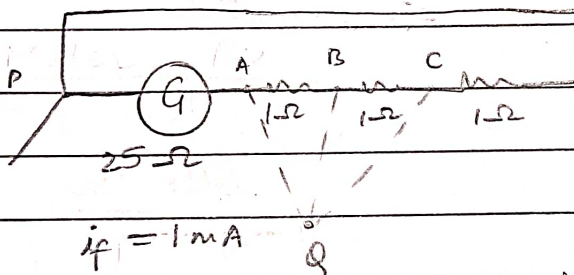QFind ranges of (A) when  $Q$  attached with A, B, C.\* (Resistance of  $Q$  & those in series with  $G$ )A.

$$i_{\text{max}} = \frac{G i_f + i_f}{S}$$

$$1. \quad i_{\text{max}} = \frac{(25)(10^{-3}) + 10^{-3}}{3} = \underline{9.3 \times 10^{-3}}$$

$$2. \quad i_{\text{max}} = \frac{(25+1)(10^{-3}) + 10^{-3}}{2} = \underline{1.4 \times 10^{-2}}$$


$$3. \quad i_{\text{max}} = \frac{(25+2)(10^{-3}) + 10^{-3}}{1} = \underline{2.8 \times 10^{-2}}$$


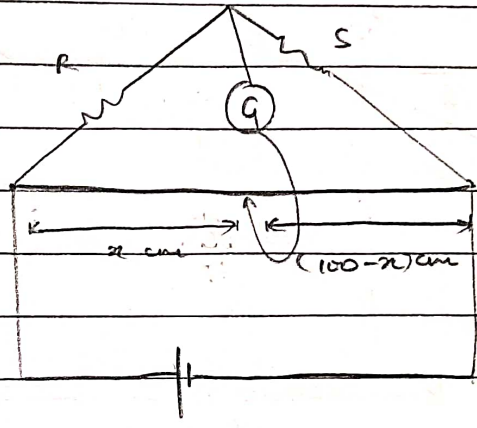
# → Meter Bridge & Post Office Box



Principle: Wheatstone Bridge

$$\frac{R}{S} = \left( \frac{x}{100-x} \right)$$



When deflection in G is zero

Meter Bridge

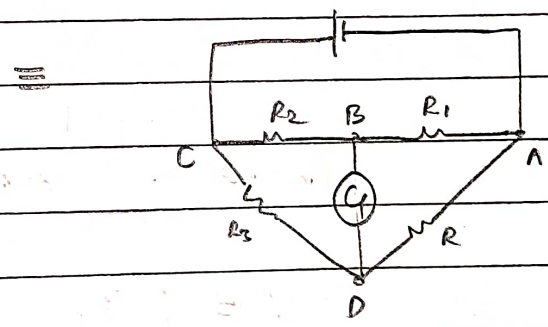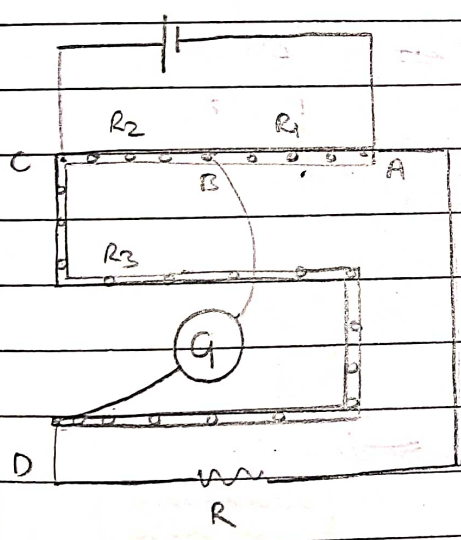


$$\frac{R_3}{R_2} = \frac{R}{R_1}$$

When deflection in G is zero
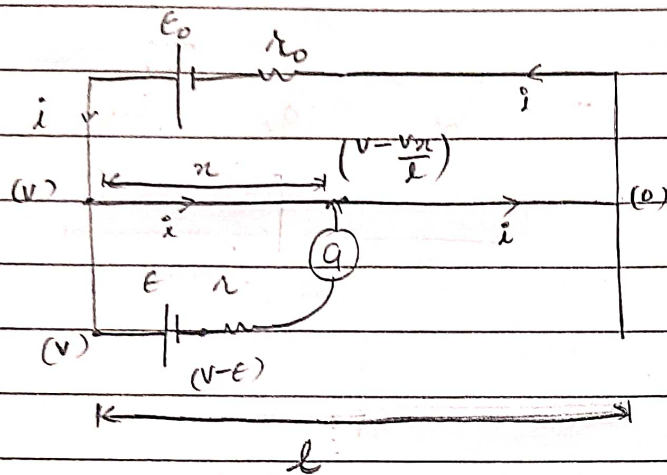
## → Potentiometer

used to find EMF & internal resistance of battery.



When deflection in  $G$  is zero.

no current through  $r$ .

$$\Rightarrow V - E = V - \frac{Vx}{l}$$

$$\Rightarrow \boxed{E = \left( \frac{Vx}{l} \right)}$$

For comparing EMF's of two batteries,

$$\boxed{\begin{array}{l} E_1 = x_1 \\ E_2 = x_2 \end{array}}$$

Here, Potential gradient =  $\left( \frac{V}{l} \right)$

$$\& \quad V = \left( \frac{E_0}{R + r_0} \right) (R) \quad \leftarrow \text{(resistance of wire)}$$

Q. If post of no deflection can't be obtained, what could be the error?


- A.
- 1) Polarity of batteries may be opposite.
  - 2)  $E > E_0$





To find  $\lambda$ , we connect a known resistance  $R$  in || to  $\lambda$ .

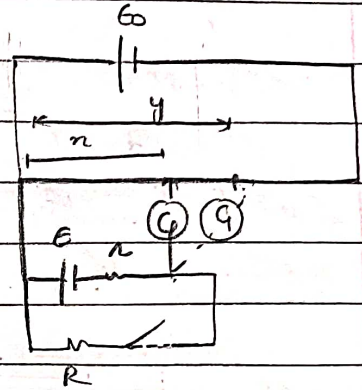We measure posts. of no deflection before & after closing the switch




$$E = \frac{Vx}{l}$$

$$E - ir = \frac{Vy}{l} \quad ; \quad i = \frac{E}{(R+x)}$$

$$\Rightarrow \left( \frac{ER}{R+x} \right) = \frac{Vy}{l}$$

$$\Rightarrow xR = y(R+x) \quad \Rightarrow \quad \lambda = \left( \frac{x-y}{y} \right) R$$


★ Q.

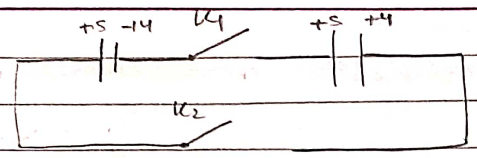

Find charge distribution when  $K_1$  closed.

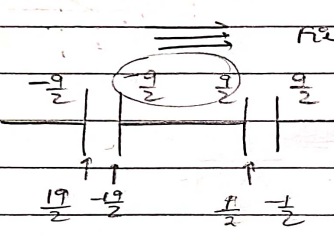
A. circuit not complete, so charge shouldn't flow.

★ (But) this happens when only insides of the plates are charged




Field created by these charges  $\Rightarrow$  Charge starts flowing.

$\Rightarrow$  Charge distr of 4 plates

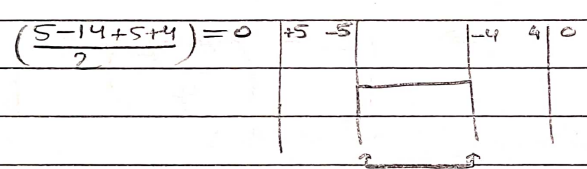

\* These are technically one plate since no charge left on outside plates  $\Rightarrow$  No E  $\Rightarrow$  same V


★ Q.

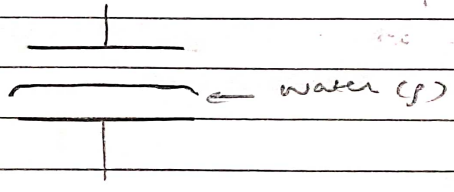

To what height does water rise if  $\sigma_0$  charge density on plates of cap.




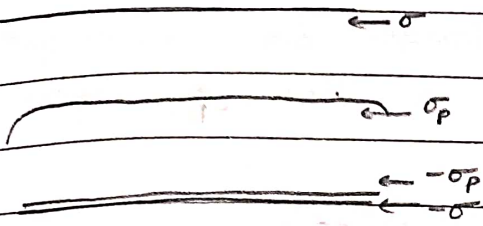A. Let charge density be  $\sigma$  at a certain inst.



$$dF = q_p dE \quad \left( \begin{array}{l} \text{E due to} \\ \text{lower plate} \end{array} \right)$$
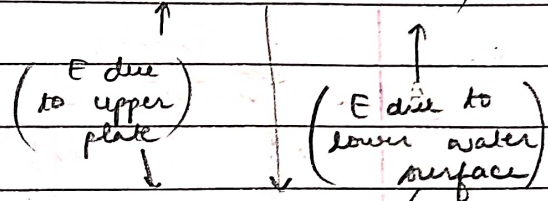
$$dF = (\sigma_p A) \left( \frac{\sigma_1 d\sigma + \sigma_2 d\sigma + \sigma_p}{2\epsilon_0} \right)$$




After time  $dt$ ,  
it changes to  
 $(\sigma + d\sigma)$ ,  
 $\sigma_p$  remaining const.

$$-(\sigma_p A) \left( \frac{\sigma + \sigma + \sigma_p}{2\epsilon_0} \right)$$

$$\Rightarrow dF = \frac{\sigma_p A}{\epsilon_0} d\sigma$$

By Q1.

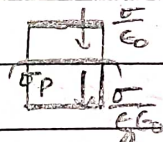

$$= \frac{A}{\epsilon_0} \left( 1 - \frac{1}{\epsilon_r} \right) \sigma d\sigma$$

$$\sigma \left( \frac{1}{\epsilon_0} - \frac{1}{\epsilon_r \epsilon_0} \right) A = \frac{\sigma_p A}{\epsilon_0}$$

$$\Rightarrow F = \frac{A}{2\epsilon_0} \left( 1 - \frac{1}{\epsilon_r} \right) \sigma_0^2$$


$$\Rightarrow \sigma_p = \sigma \left( 1 - \frac{1}{\epsilon_r} \right)$$

This force will balance the wt. of risen water,

$$\Rightarrow F = mg = \rho g h A$$

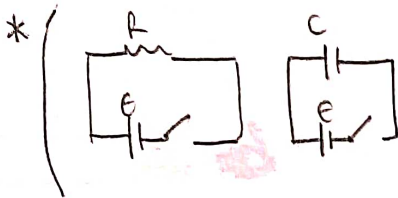
$$\Rightarrow h = \frac{(\epsilon_r - 1) \sigma^2}{2\epsilon_0 \rho g}$$






when switch closed, current experiences  
impulsive force  $\Rightarrow$  Energy conservation cannot be used.  
 ag.  $q = CE$   $W_{\text{battery}} = qV = CE^2$   
 $U_{\text{cap}} = \frac{1}{2}CE^2$   $\Rightarrow$  Energy lost as heat

Q.

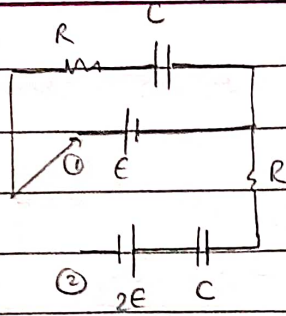

Initially steady state.  
 At  $t=0$ , switch shifted from ① to ②.  
 Find charge on uncharged cap. as a fun of time.

A.

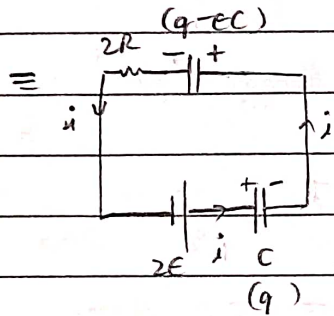

(ML)  $2E - \frac{q}{C} - \left(\frac{q-EC}{C}\right) - 2Ri = 0$   
 $\Rightarrow 2E - \frac{2q}{C} + E = 2R \frac{dq}{dt}$   
 $\Rightarrow 2R \frac{dq}{dt} + \frac{2q}{C} = 3E$

$i = \frac{dq}{dt}$


$\Rightarrow q = (3E) \left(\frac{C}{2}\right) \left(1 - e^{-\frac{t}{RC}}\right)$

\* Q

Each plate of a parallel plate capacitor has area 'A'. Find amt. of work done to  $\uparrow$  the distance of plates from  $x_1$  to  $x_2$ , keeping voltage across capacitor to be const. 'V'.

A.

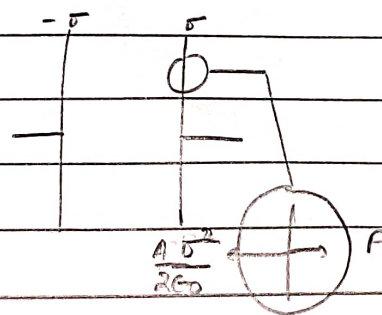\* Whenever battery attached, Energy conservation cannot be used.  
 so we need to use force.



for moving slowly,  
 $V = \frac{\sigma x}{\epsilon_0}$

$F = \frac{A\sigma^2}{2\epsilon_0} = \frac{V^2 A \epsilon_0}{2x^2}$

$dW = F \cdot dx = \frac{V^2 A \epsilon_0}{2} \frac{dx}{x^2}$

$W = \int_{x_1}^{x_2} dW = \left(\frac{V^2 A \epsilon_0}{2}\right) \left(\frac{1}{x_1} - \frac{1}{x_2}\right)$